

Linear Circuits

BONNIE FERRI, PROFESSOR AND ASSOCIATE CHAIR
School of Electrical and Computer Engineering




Module 2

Lesson 2: Kirchhoff's Current Law


Kirchhoff's Current Law

Builds Upon:

- Ohm's Law ($V=iR$)

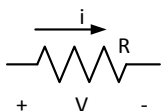


- Nodes

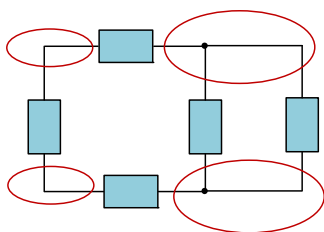

Kirchhoff's Current Law (KCL)

Sum of the currents leaving a node =
sum of current entering the node
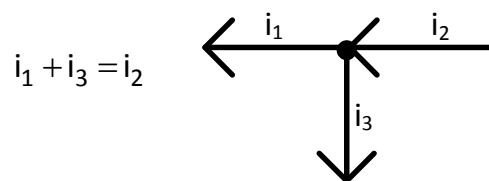
$$\sum i_{\text{leaving}} = \sum i_{\text{entering}}$$




Kirchhoff's Current Law (KCL)

Sum of the currents leaving a node =
sum of current entering the node

$$\sum i_{\text{leaving}} = \sum i_{\text{entering}}$$

$$i_1 + i_3 = i_2$$

$$i_1 + i_3 - i_2 = 0$$

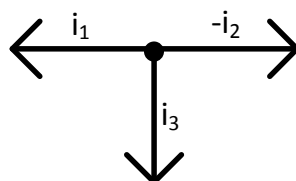


Kirchhoff's Current Law (KCL)

Sum of the currents leaving a node = zero

$$\sum i_{\text{leaving}} = 0$$


$$i_1 + i_2 + i_4 = 0$$

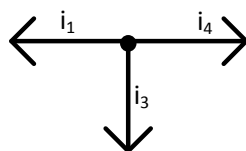


Sum of the currents entering a node = zero

$$\sum i_{\text{entering}} = 0$$

$$i_2 + i_5 + i_6 = 0$$

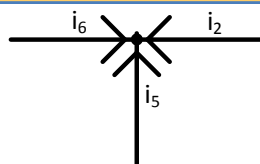


KCL For Series Elements

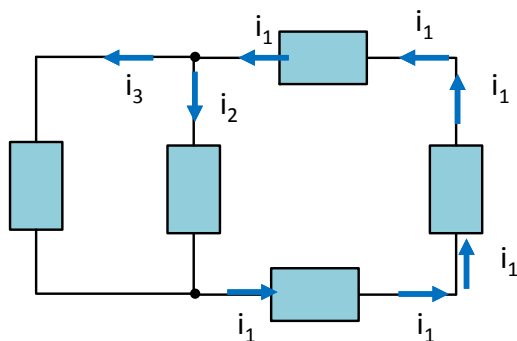

The current is the same through series elements.

KCL Example and Quiz

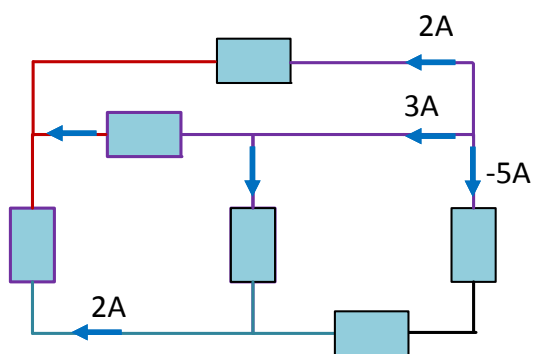


$$\sum i_{\text{leaving}} = 0$$


$$\sum i_{\text{entering}} = 0$$

$$\sum i_{\text{leaving}} = \sum i_{\text{entering}}$$


KCL Example and Quiz

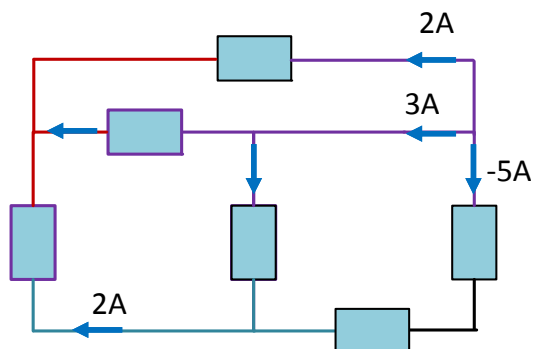

KCL and KVL Example

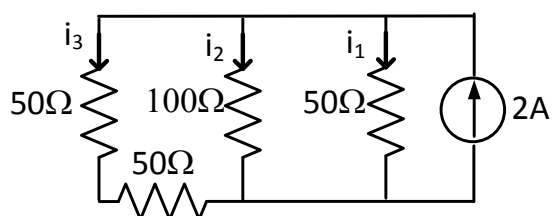

Key Concepts

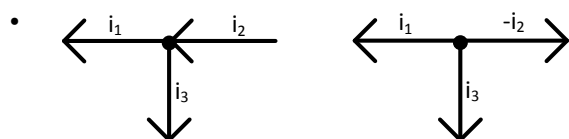


- KCL:

$$\sum i_{\text{leaving}} = \sum i_{\text{entering}}$$

$$\sum i_{\text{leaving}} = 0 \quad \sum i_{\text{entering}} = 0$$

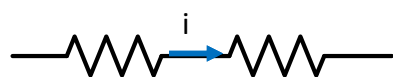- Series components have the same current



- Solve problems by combining KVL and KCL