



# Linear Circuits

BONNIE FERRI, PROFESSOR AND ASSOCIATE CHAIR  
School of Electrical and Computer Engineering




## Module 2

### Lesson 5: Voltage Divider Law

# Voltage Divider Law


Objective:


- Be able to use

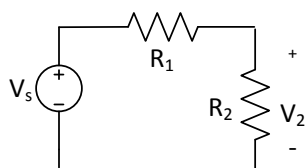


Voltage Divider Law

## Builds Upon:

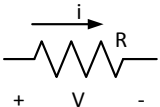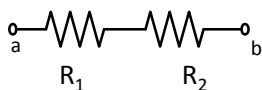
- Ohm's Law:  $V=iR$  
- Resistors in series:  $R_{eq} = R_1 + R_2$




## Voltage Divider Law

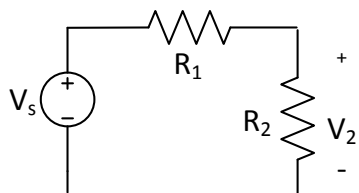




$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$

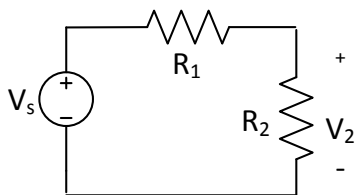


$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$

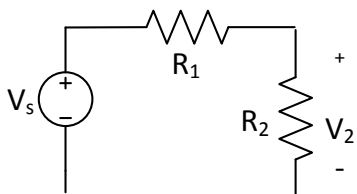**Voltage Divider Law Quiz**

What is  $V_2$  if  $V_s = 10\text{V}$  and  $R_1 = 200\Omega$  and  $R_2 = 200\Omega$  ?

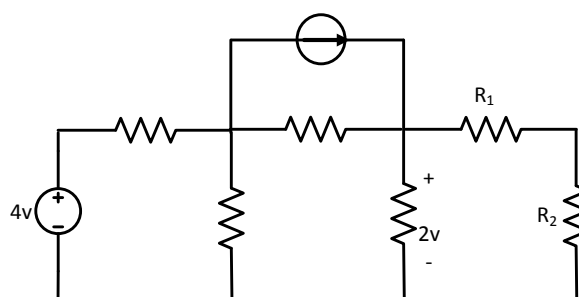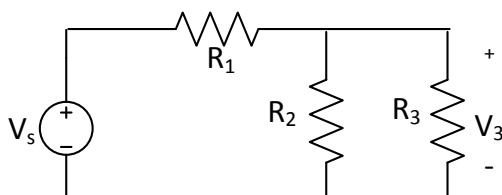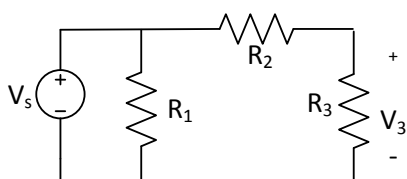**Recognize When to use Voltage Divider Law**


## Voltage Divider Quiz

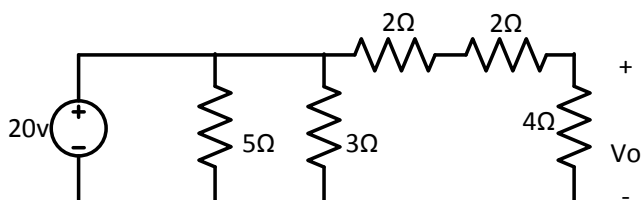

What is  $V_o$ ?

## Key Concept

- Voltage Divider Law

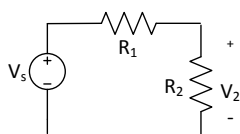

$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$