



Linear Circuits

BONNIE FERRI, PROFESSOR AND ASSOCIATE CHAIR
School of Electrical and Computer Engineering




Module 2

Lesson 4: Equivalent Resistance

Equivalent Resistance


Objective:

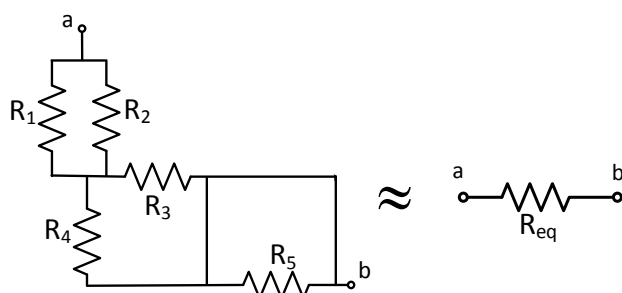- Simplify a combinations of resistors by replacing them with equivalent resistors




Builds Upon

- Resistors in Series:


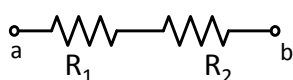


$$R_{eq} = \sum R_k$$




- Resistors in Parallel:

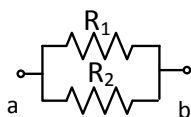


$$R_{eq} = \frac{1}{\sum \frac{1}{R_k}}$$

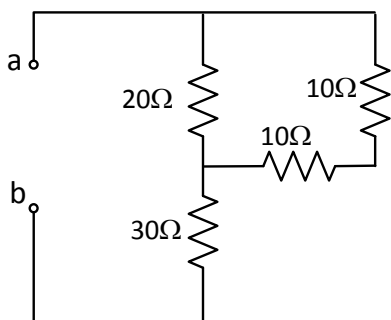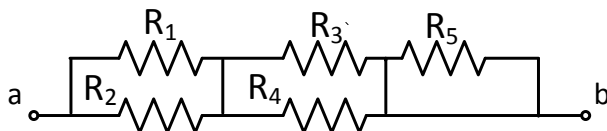Example**Example**

Example

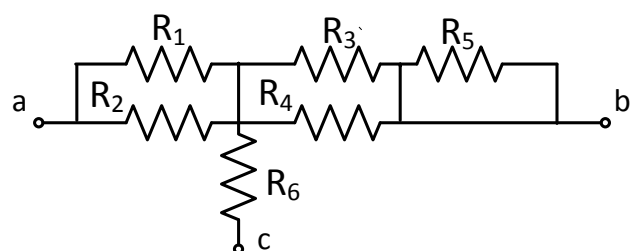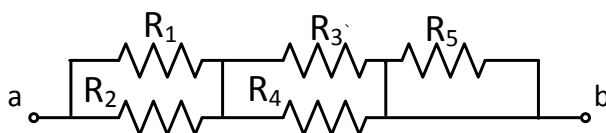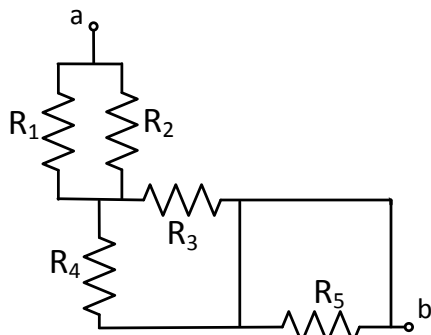

Example

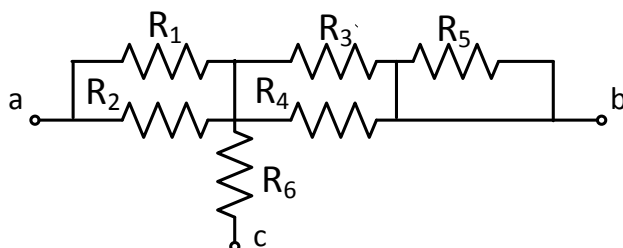

Key Concept

- Replace series and parallel resistor combinations with their equivalent resistances
- Redraw and reduce again, down to one resistor