



Linear Circuits

BONNIE FERRI, PROFESSOR AND ASSOCIATE CHAIR
School of Electrical and Computer Engineering



Module 2


Lesson 3: Series and Parallel Resistance

Series and Parallel Resistors


Objective:

- Simplify combinations


Series

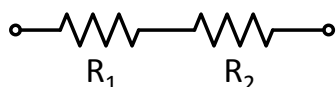

Parallel

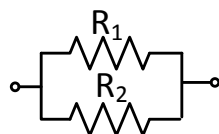


Builds Upon:

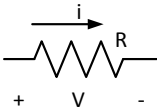
- Ohm's Law: $V=iR$ 
- KCL: $\sum i_{\text{leaving}} = 0$
- KVL: $\sum v_{\text{loop}} = 0$

Equivalent Resistance


Series

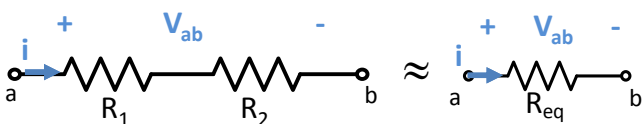

Parallel

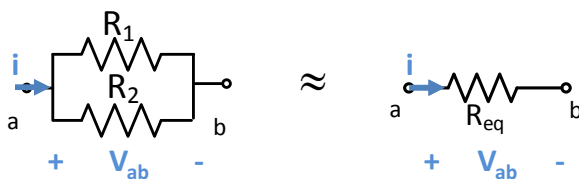

Resistors in Series

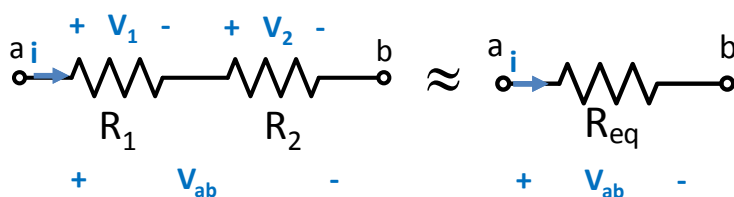

$$R_{eq} = R_1 + R_2$$

$$V_{ab} = V_1 + V_2$$


$$V_{ab} = R_1 i + R_2 i$$

$$V_{ab} = (R_1 + R_2) i$$


Resistors in Series

- K resistors in series: $R_{eq} = \sum R_k$


- Example:

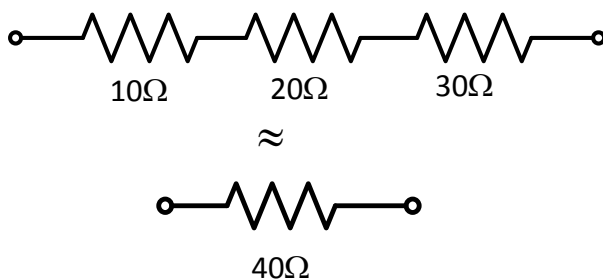

Resistors in Parallel

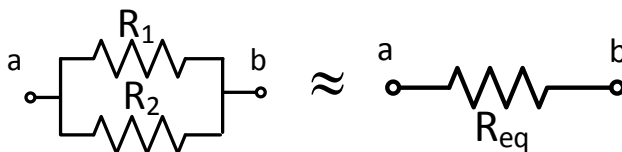

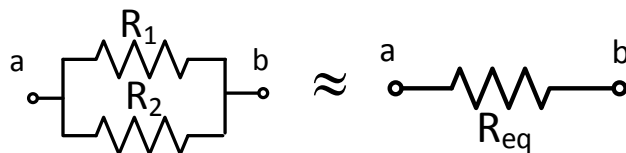
$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$



$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

Resistors in Parallel

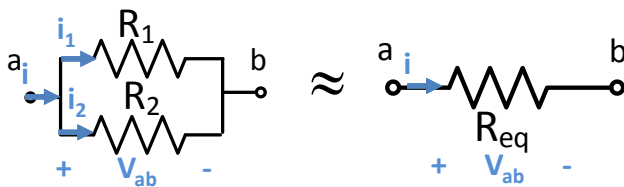

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{KCL: } i = i_1 + i_2 \Rightarrow i_1 = i - i_2$$

$$\text{KVL: } V_{ab} = R_1 i_1 = R_2 i_2$$

$$R_1(i - i_2) = R_2 i_2 \Rightarrow i_2 = \frac{R_1}{R_1 + R_2} i$$


$$\text{KVL: } V_{ab} = R_2 i_2$$

$$V_{ab} = R_2 \frac{R_1}{R_1 + R_2} i$$

Resistors in Parallel

- Shorted resistors:




$$R_{eq} = 0$$

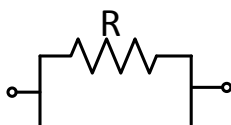

- K resistors in parallel:

$$R_{eq} = \frac{1}{\sum \frac{1}{R_k}}$$

Examples

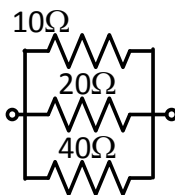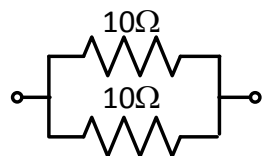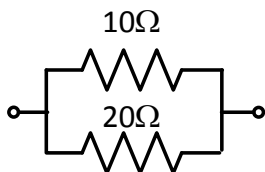

Key Concepts

- Resistors in Series:

$$R_{eq} = \sum R_k$$

- Resistors in Parallel:

$$R_{eq} = \frac{1}{\sum \frac{1}{R_k}}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

- $R_{eq} = 0$ for a short circuit in parallel with a resistor